

## Circuit Diagram

Consist of Arduino Uno R3, Photoresistor, 1 k $\Omega$  Resistor , Light bulb, Power Supply, NPN Transistor (BJT)

